

## Maths reminder for Electrochemists

### Part II: The simplicity of Laplace transform

#### I – INTRODUCTION

Several electrochemical techniques use results obtained using the Laplace transform. Examples can be found in Application notes #21, #28, #38 and #41b [1-4].

#### I - 1 DEFINITIONS

The Laplace<sup>1</sup> transform of a function  $f(t)$  is defined by the integral

$$F(s) = \mathcal{L}\{f(t)\} = \int_0^{\infty} f(t) \exp(-st) dt \quad (1)$$

Where  $s$  is the Laplace complex variable [5]. For example the Laplace transform of the sine function  $\sin(t)$  is given by

$$\int_0^{\infty} \sin(t) \exp(-st) dt \quad (2)$$

On the other hand, the time function is given by a more complicated expression from the Laplace transform in the  $s$ -domain by

$$\begin{aligned} f(t) &= \mathcal{L}^{-1}\{F(s)\} \\ &= \frac{1}{2\pi i} \lim_{T \rightarrow \infty} \int_{\gamma-iT}^{\gamma+iT} \exp(st) F(s) ds \end{aligned} \quad (3)$$

#### I - 2 TABLE OF LAPLACE TRANSFORMS

Calculation of the integral of a function of a real variable is sometimes easy, e.g. it is well known that  $\int x dx = x^2/2$ . Calculation of the integral of a function of a complex variable is much more difficult. Fortunately it is very rare to have to use Eqs. (1) or (3). Laplace transforms and inverse Laplace transforms usually used in electrochemistry have already been calculated. The result is obtained by

consulting a table of Laplace transform [5] (Tabs. I and II), or better using a software such as Wolfram Alpha [6].

#### II – TRANSFER FUNCTION OF A LINEAR AND TIME INVARIANT (LTI) SYSTEM

##### II - 1 DEFINITION

Laplace transform is the tool of choice for the study of linear and time invariant systems (Fig. 1) characterized by their transfer function  $H(s)$  defined by [7, 8]

$$H(s) = \frac{Y(s)}{X(s)} = \frac{\mathcal{L}\{y(t)\}}{\mathcal{L}\{x(t)\}} \quad (4)$$

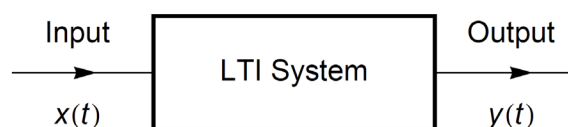


Figure 1: Sketch of a scalar dynamic system.

For example, the impedance of a dipole is the transfer function for a current input

$$Z(s) = \frac{\mathcal{L}\{\Delta E(t)\}}{\mathcal{L}\{\Delta I(t)\}} = \frac{\Delta E(s)}{\Delta I(s)} \quad (5)$$

With  $\Delta E(t) = E(t) - E_{t=0}$  and  $\Delta I(t) = I(t) - I_{t=0}$ .

#### III – RESPONSE OF A LTI SYSTEM

##### III - 1 INTRODUCTION

Knowing the transfer function of a system allows us to calculate its response to an input. For example, if  $Z(s)$  is known, it is possible to determine the response of the dipole in the Laplace domain

$$\Delta E(s) = \Delta I(s) Z(s) \quad (6)$$

<sup>1</sup> Pierre-Simon Laplace was a French mathematician of the eighteenth century (1749-1827).

Then in the time domain using inverse Laplace transform

$$\Delta E(t) = \mathcal{L}^{-1} \{ \Delta E(s) \} \quad (7)$$

### III - 2 RESPONSE OF A PARALLEL RC CIRCUIT TO A CURRENT HEAVISIDE STEP FUNCTION



#### a. Impedance of a parallel RC circuit

The impedance of a parallel RC circuit is directly written from the admittance  $Y(s) = 1/Z(s)$  [9]:

$$Y(s) = \frac{1}{R} + sC \Rightarrow Z(s) = \frac{R}{1 + RCs} \quad (8)$$

#### b. Response to a Heaviside step function

The Heaviside step function is equal to 0 for  $t < 0$  and 1 for  $t > 0$  (Fig. 2). The Laplace transform of the Heaviside step function is given by (Tab. I, Eqs. (1) and (2)).

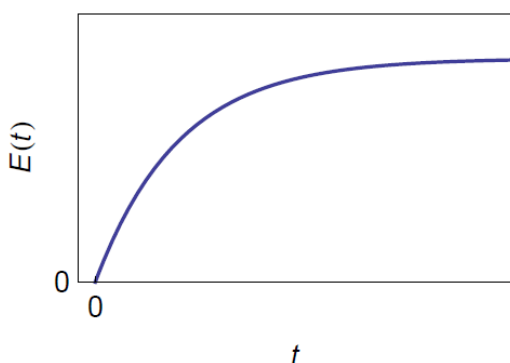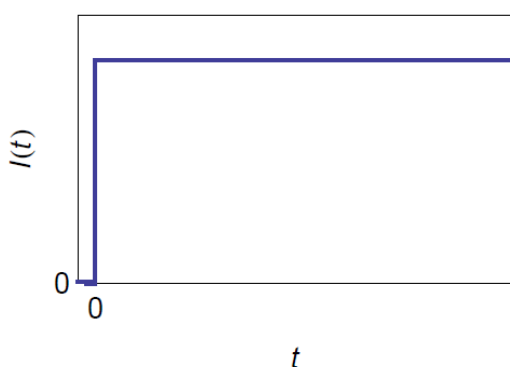

**Figure 2: Potential response of the parallel RC circuit to a Heaviside step current using Eq. (11).**

$$\Delta I(s) = \mathcal{L} \{ \delta I(t) \} = \frac{\delta I}{s} \quad (9)$$

The Laplace transform of the output is written

$$\Delta E(s) = \frac{\delta I}{s} \frac{R}{1 + RCs} \quad (10)$$

And the time domain response is given by (Tab. II, Eqs. (1) and (2)):

$$\begin{aligned} \Delta E(t) &= \mathcal{L}^{-1} \{ \Delta E(s) \} = \mathcal{L}^{-1} \left\{ \frac{\delta I}{s} \frac{R}{1 + RCs} \right\} \\ &= \delta IR \left( 1 - \exp\left(\frac{-t}{CR}\right) \right) \end{aligned} \quad (11)$$

#### c. Response to a sinusoidal input

The Laplace transform of a sinusoidal signal is given by (Tab. I, Eqs (1) and (4))

$$I(t) = \delta I \sin(\omega t) \Rightarrow I(s) = \mathcal{L} \{ \delta I(t) \} = \frac{\delta I \omega}{s^2 + \omega^2} \quad (12)$$


Therefore the output potential in the Laplace domain is

$$\Delta E(s) = \frac{\delta I \omega}{s^2 + \omega^2} \frac{R}{1 + RCs}$$

And the time domain response is given by (Tab. II, Eqs. (1) and (4))

$$\begin{aligned} \Delta E(t) &= \mathcal{L}^{-1} \{ \Delta E(s) \} = \mathcal{L}^{-1} \left\{ \frac{\delta I \omega}{s^2 + \omega^2} \frac{R}{1 + \tau s} \right\} \\ &= \frac{\delta IR \left( \tau \omega \exp\left(\frac{-t}{\tau}\right) - \tau \omega \cos(\omega t) + \sin(\omega t) \right)}{1 + \tau^2 \omega^2} \end{aligned} \quad (13)$$

With  $\tau = RC$ . The establishment of the sinusoidal steady-state of potential is shown in Fig. 3.

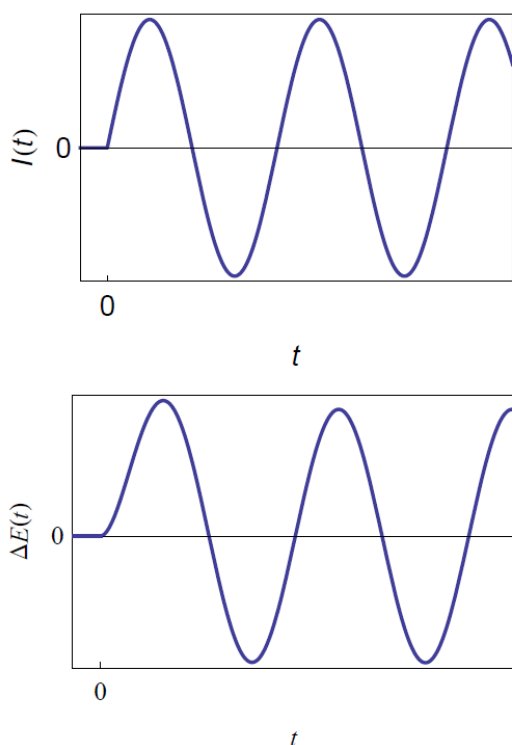

**Figure 3:** Potential response of the parallel RC circuit to a sinusoidal current using Eq. (13).

### III - 3 RAMP RESPONSE OF A SERIES RC CIRCUIT

#### a. Impedance of a series RC circuit

The impedance of a series RC circuit is given by

$$Z(s) = R + \frac{1}{C_s} \quad (14)$$

#### b. Response to a potential ramp

The signal used in linear sweep voltammetry is a potential ramp defined as:

$$E(t) = E_i + vt \Rightarrow \Delta E(t) - E_i = vt \quad (15)$$

The Laplace transform of a ramp is given by (Tab I., Eqs. (1) and (3))

$$\Delta E(s) = L \{ \Delta E(t) \} = L \{ vt \} = \frac{v}{s^2} \quad (16)$$

With


$$Z(s) = \frac{\Delta E(s)}{\Delta I(s)} \Rightarrow \Delta I(s) = \frac{\Delta E(s)}{Z(s)}$$

It is obtained

$$\Delta I(t) = L^{-1} \{ \Delta I(s) \} = L^{-1} \left\{ \frac{Cv}{s(1+CRs)} \right\}$$

And using Eqs. (1) and (2) (Tab. II),

$$\Delta I(t) = I(t) = Cv \left( 1 - \exp\left(\frac{-t}{RC}\right) \right) \quad (17)$$

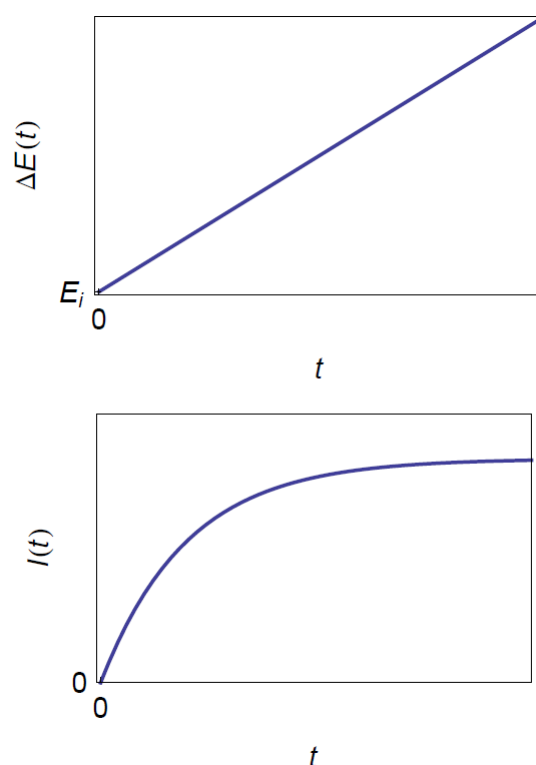

**Figure 4:** Current response of the serie RC circuit to a ramp of potential calculated using Eq. (17).

## IV – LAPLACE AND INVERSE LAPLACE TRANSFORMS TABLES

### IV - 1 LAPLACE TRANSFORMS

Laplace transforms used in this note are shown in Tab. I.

**Table I: Table of Laplace transforms.**

	$f(t)$	$F(s)$
(1)	$a f(t)$	$a F(s)$
(2)	1	$\frac{1}{s}$
(3)	$t$	$\frac{1}{s^2}$
(4)	$\sin(\omega t)$	$\frac{\omega}{s^2 + \omega^2}$

### IV - 2 INVERSE LAPLACE TRANSFORMS

Inverse Laplace transforms used in this note are shown in Tab. II.

**Table II: Table of inverse Laplace transforms.**

	$F(s)$	$f(t)$
(1)	$a F(s)$	$a f(t)$
(2)	$\frac{1}{s(1 + as)}$	$1 - \exp(-t/a)$
(3)	$\frac{1}{s^2(1 + as)}$	$a(\exp(-t/a) - 1) + t$
(4)	$\frac{1}{(1 + as)(1 + bs^2)}$	$\frac{a \exp(-t/a) - a \cos\left(\frac{t}{\sqrt{b}}\right) + \sqrt{b} \sin\left(\frac{t}{\sqrt{b}}\right)}{a^2 + b}$

## REFERENCES

- 1) [Application note #21](#) "Measurement of the double layer capacitance"
- 2) [Application note #28](#) "Ohmic drop. Part II: Introduction to Ohmic Drop measurement techniques."
- 3) [Application note #38](#) "Dynamic resistance determination. A relation between AC and DC measurement?"
- 4) [Application note #41 II](#) "CV Sim, Simulation of the simple redox reaction (E), Part II: The effect of the ohmic drop and the double layer capacitance."
- 5) [http://en.wikipedia.org/wiki/Laplace\\_transform](http://en.wikipedia.org/wiki/Laplace_transform).
- 6) Wolfram Alpha: Computational Knowledge Engine. <http://www.wolframalpha.com>.
- 7) [http://en.wikipedia.org/wiki/Transfer\\_function](http://en.wikipedia.org/wiki/Transfer_function).
- 8) [Handbook of EIS](#) - Transfer functions.
- 9) [Handbook of EIS](#) - Circuits made of resistors and capacitors.

*Revised in 07/2018*